

JNANAPEETA DCET ACADEMY

LETS DREAM IT.

Fundamentals of Electrical & Electronics Engineering (20EE01P/20EC01P)

Unit-2 ELECTRICAL FUNDAMENTALS (SESSION-4)

Topics:

- Relation between voltage, current and resistance (Ohm's Law)
- Behaviour of V, I in series and parallel DC circuits
- Open circuit, closed circuit and short circuit

4.1 Ohms Law:

Ohm's law states that the current flowing through a conductor is directly proportional to the potential difference (voltage) between two points of a conductor provided the temperature and other parameters remains constant

i.e.


$$V \propto I$$

$$V = I \cdot R$$

where, V = Voltage
I = Current
R = Resistance

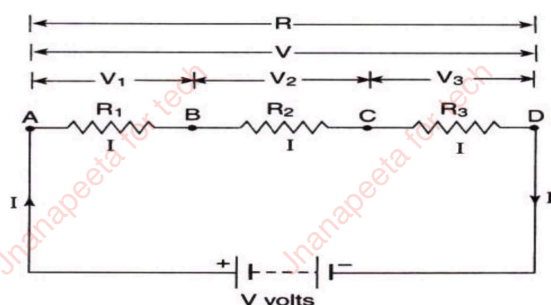4.2.1 Behavior of V, I in Series DC circuit:

In series circuit resistances are connected end to end like a chain. In DC series circuit the emf source is battery.



Characteristics of series circuit:

- Voltage drops add to equal total voltage.
- All components share the same (equal) current.
- Resistances add to equal total resistance.
- Example for series circuit is "serial light set"

Fig. shows three resistances R1, R2 and R3 Connected in series with a battery of V volts. Let the p.d. across R1, R2 and R3 is V1, V2 and V3 respectively. Total voltage across the combination divides among each resistance. The total voltage is given by,

JNANAPEETA DCET ACADEMY

LETS DREAM IT.

Fundamentals of Electrical & Electronics Engineering (20EE01P/20EC01P)

$$V = V_1 + V_3 + V_2;$$


The total resistance is given by,

$$R = R_1 + R_2 + R_3;$$

The effective resistance of resistances connected in series is the sum of individual resistances.

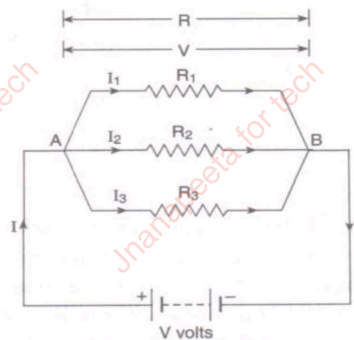4.2.2. Behaviour of V, I in Parallel DC circuit:

The resistances are said to be connected in parallel, if first end of all resistances are connected to a common point and other ends of resistances are connected to another common point.



- All components share the same (equal) voltage.
- Branch currents add to equal total current.
- Resistances diminish to equal total resistance.
- Example for parallel circuit is – all appliances, lamps in home are connected in parallel.

If I is the total current flowing in the circuit, then the current passing through resistance R_1 (branch 1) is I_1 , current passing through resistance R_2 (branch 2) is I_2 and current passing through resistance R_3 (branch 3) is I_3 .

$$\text{Total current } I = I_1 + I_2 + I_3 ;$$

Effective resistance R is given by (explained in the next session)

$$1/R = 1/R_1 + 1/R_2 + 1/R_3;$$

JNANAPEETA DCET ACADEMY

LETS DREAM IT.

Fundamentals of Electrical & Electronics Engineering (20EE01P/20EC01P)

4.3 Open circuit, Closed circuit and Short Circuit:

Open circuit: An electrical circuit in which the continuity is broken so that current does not flow.

Closed circuit: a circuit without interruption, providing a continuous path through which a current can flow.

Short Circuit: A low-resistance connection between two points in an electric circuit through which the current tends to flow rather than along the intended path. A short circuit can damage the circuit by overheating.

